

3.5: Corrente elétrica e DC

$$1) A = 7,0 \text{ cm}^2$$

$$V = A \times h$$

Ag⁺ N₂O₃

$$= 7 \times 10^{-4} \times 0,133 \times 10^{-3}$$

$$V = 12 \text{ V}$$

$$= 9,31 \times 10^{-8} \text{ m}^3$$

$$R = 1,8 \Omega$$

$$l = 0,133 \text{ mm}$$

$$\rho = 10,5 \times 10^3 \text{ kg/m}^3$$

$$m_{\text{Ag}} = \rho V = 10,5 \times 10^3 \times 9,31 \times 10^{-8} = 9,78 \times 10^{-4} \text{ kg}$$

$$m = 107,87 \text{ g/lunde}$$

nº de átomos da prata:

$$N = 9,78 \times 10^{-4} \times \frac{6,02 \times 10^{23}}{107,87 \times 10^{-3}} = 5,46 \times 10^{21} \text{ átomos}$$

$$I = \frac{V}{R} \quad (\Rightarrow) \quad I = \frac{12}{1,8} = 6,67 \text{ A (C/s)}$$

$$\Delta t = \frac{\Delta Q}{I} = \frac{N e}{I} = \frac{5,46 \times 10^{21} \times 1,60 \times 10^{-19}}{6,67} = 131 \text{ s}$$

$$2) I(t) = I_0 e^{-\frac{t}{T}}$$

$$(dq = I dt)$$

$$a) t=0 \text{ e } t=T$$


$$Q(t) = \int_0^t I_0 e^{-\frac{t}{T}} dt = I_0 \left[-T e^{-\frac{t}{T}} \right]_0^t \\ = I_0 \left(-T \right) \left[e^{-\frac{t}{T}} - 1 \right] \\ = + I_0 T \left[1 - e^{-\frac{t}{T}} \right]$$

$$\text{Logo, } t=T \Rightarrow Q(T) = I_0 T (1 - e^{-1}) \text{ C}$$

$$b) Q(10T) = I_0 T (1 - e^{-10}) \text{ e}$$

$$c) \lim_{t \rightarrow \infty} Q(t) = I_0 T (1 - e^{-\infty}) = I_0 T$$

3)

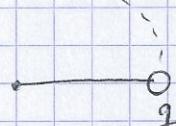

$$I = \frac{Q}{T}$$

$$\omega = \frac{2\pi}{T} \quad (\Rightarrow) \quad T = \frac{2\pi}{\omega} \quad (\Delta)$$

ω

$I = ?$

$$\text{Logo} \quad I = \frac{q}{\frac{2\pi}{\omega}} = \frac{q\omega}{2\pi}$$

4)



$$\omega = 2\pi f$$

$$I = \frac{Q}{T} = \frac{Q}{\frac{2\pi}{\omega}} = \frac{Q\omega}{2\pi}$$

5) $l = 1,5 \text{ m}$

$$I = \frac{\Delta V}{R} = \frac{0,90}{R}$$

$$A = 0,60 \text{ mm}^2$$

$$\Delta V = 0,90 \text{ V}$$

$$R = \frac{L}{\sigma A} = \frac{1}{\sigma} \cdot \frac{L}{A} = \rho \frac{L}{A} = 5,6 \times 10^8 \times \frac{1,5}{0,60 \times 10^{-6}}$$

$$\rho = 5,6 \times 10^8 \text{ Ohm}$$

$$\Rightarrow R = 0,14 \Omega$$

$$\text{Daraus } I = \frac{0,90}{0,14} = 6,43 \text{ A}$$

6)



$$m = 90,0 \text{ g}$$

$$\rho_v = 10,5 \text{ g/cm}^3$$

$$\text{a) } R = \rho \frac{L}{A} = \rho \frac{l}{l^2} = \frac{\rho}{l}$$

$$\text{Setze ein und } R_v = \frac{m}{V} \Rightarrow$$

$$\Rightarrow l^3 = \frac{m}{\rho_v} \Rightarrow l = \sqrt[3]{\frac{90 \times 10^{-3}}{10,5 \times 10^{-3}}} \Rightarrow l = 2,05 \text{ cm}$$

$$\text{Tabelle: } \rho = 1,59 \times 10^{-8} \text{ Ohm.m}$$

$$\text{Daraus } R = \frac{1,59 \times 10^{-8}}{2,05 \times 10^{-2}} = 7,76 \times 10^{-7} \Omega \quad (\text{umfassend!})$$

b) $I_e \rightarrow L \text{ ändern}$

$$I = nqAv$$

$$V = 10,0 \text{ mV}$$

$n \rightarrow \text{nº eletrôns/m}^3$
 $q \rightarrow \text{carga elementar}$
 $v \rightarrow \text{velocidade média}$

$$I = \frac{\Delta V}{R} = \frac{10 \times 10^{-3}}{7,76 \times 10^{-7}} = 1,29 \times 10^4 \text{ A}$$

$$1 \text{ cm}^3 = (10^{-2})^3 = 10^{-6} \text{ m}^3$$

$$n = \frac{10,5 \times 10^6}{107,87} \times 6,02 \times 10^{23} = 5,86 \times 10^{28} \text{ eletrôns/m}^3$$

$$v = \frac{I}{nqA} = \frac{1,29 \times 10^4}{5,86 \times 10^{28} \times 1,60 \times 10^{-19} \times (2,05 \times 10^{-2})^2}$$

$$= 3,25 \times 10^{-3} \text{ m/s}$$

②


7) R

$$l' = 1,25l$$

$$R = \rho \frac{l}{A}$$

$$R' = \rho \frac{1,25l}{(A/1,25)} = 1,25^3 \rho \frac{l}{A} = 1,56 R$$

a)

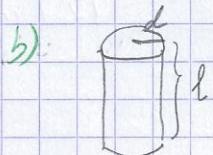

$$R = \frac{\rho l}{\pi r^2} \Leftrightarrow \pi r^2 = \frac{\rho l}{R}$$

$$\Leftrightarrow r = \sqrt{\frac{\rho l}{\pi R}} \Leftrightarrow d = 2 \sqrt{\frac{\rho l}{\pi R}}$$

8)

cavão
níquel

$$\rho_c = 3,5 \times 10^{-8} \Omega \cdot m$$

$$\rho_n = 1,50 \times 10^{-6} \Omega \cdot m$$

$$R = 10 \Omega$$

$$R = \rho \frac{l}{A} = \rho(T) \frac{l}{A}$$

$$\text{Série} \quad R = R_c + R_n$$

$$= \rho_0 [1 + \alpha(T - T_0)] \frac{l}{A}$$

$$R_c = R_c [1 + 0,5 \times 10^{-3}(T - T_0)]$$

$$R_n = R_n [1 + 0,4 \times 10^{-3}(T - T_0)]$$

$$R_c + R_n = R_c - 0,5 \times 10^{-3} R_c (T - T_0) + R_n + 0,4 \times 10^{-3} R_n (T - T_0)$$

$$0,5 \times 10^{-3} R_c (T - T_0) = 0,4 \times 10^{-3} R_n (T - T_0)$$

$$R_c = 0,8 R_n$$

Logo,

$$R = R_c + R_n = 1,8 R_n$$

$$R_n = \frac{10 \times 10^3}{1,8} = 5,56 \times 10^3 \Omega$$

$$\Rightarrow R_c = 10 \times 10^3 - 5,56 \times 10^3 = 4,44 \times 10^3 \Omega$$

$$9) R = 1,00 \Omega \rightarrow 20^\circ C \quad R = R_0 (1 + \alpha(T - T_0))$$

$$-196^\circ C$$

$$R = 1 (1 + 3,92 \times 10^{-3} (-196 - 20))$$

$$\alpha = 3,92 \times 10^{-3} \frac{1}{K}$$

$$R = 0,15 \Omega //$$

$$10) P=500 \text{ W}$$

$$a) T_0 = 20^\circ\text{C}$$

$$I = \frac{\Delta V}{R}$$

$$\Delta V = 220 \text{ V}$$

$$P = I \Delta V = \frac{(\Delta V)^2}{R} \quad (\Rightarrow)$$

$$d = 0,5 \text{ mm}$$

$$\downarrow \\ r = 0,25$$

$$(\Rightarrow) R = \frac{220^2}{500} = 96,8 \Omega$$

$$R = \frac{\rho l}{A} \quad (\Rightarrow) \quad l = \frac{AR}{\rho} = \frac{\pi \times (0,25 \times 10^{-3})^2 \times 96,8}{1,50 \times 10^{-6}} = 12,7 \text{ m}$$

$$b) T = 1200^\circ\text{C}$$

$$R = R_0 [1 + \alpha (T - T_0)]$$

$$= 96,8 [1 + 0,4 \times 10^{-3} \times 1180] = 142,5 \Omega$$

$$\log, \quad P = \frac{220^2}{142,5} = 339,6 \text{ W}$$

$$11) l = 25 \text{ m}$$

$$a) \Delta V = El \quad (\Rightarrow) E = \frac{\Delta V}{l} = \frac{I R}{l} =$$

$$d = 0,4 \text{ mm}$$

$$T_0 = 20^\circ\text{C}$$

$$I = 0,5 \text{ A}$$

$$= \frac{I \cdot \rho \frac{l}{A}}{l} = \frac{I \rho}{A} =$$

$$= \frac{0,5 \times 1,50 \times 10^{-6}}{\pi \times (0,2 \times 10^{-3})^2} = 5,97 \text{ V/m}$$

$$b) P = I \cdot \Delta V = I \cdot IR = I^2 \cdot \rho \cdot \frac{l}{A} = 0,5^2 \times 1,50 \times 10^{-6} \times \frac{25}{\pi (0,2 \times 10^{-3})^2} = \\ = 74,6 \text{ W}$$

$$c) T = 340^\circ\text{C}$$

$$R = R_0 [1 + \alpha (T - T_0)]$$

$$\Delta V =$$

$$R = 1,50 \times 10^{-6} \times \frac{25}{\pi (0,2 \times 10^{-3})^2} [1 + 0,4 \times 10^{-3} \times 320]$$

$$R = \frac{298,42}{R_0} \times 1,128 = 336,62 \Omega$$

$$P = \frac{(\Delta V)^2}{R}$$

$$\text{mas } \Delta V = I_0 R_0 = 0,5 \times 298,42 = 149,21$$

$$= \frac{149,21^2}{336,62} = 66,14 \text{ W}$$

(3)

$$12) \text{ niquel } R = 1,50 \times 10^{-6} \Omega \cdot \text{m} \quad \alpha = 0,4 \times 10^{-3}$$

$$\Delta V = 120 \text{ V}$$

$$T_0 = 20^\circ\text{C}$$

$$I_0 = 1,8 \text{ A} \quad - I_1 = 1,53 \text{ A}$$

$$a) \quad P = I \Delta V = 1,53 \times 120 = 183,6 \text{ W}$$

$$b) \quad R = R_0 (1 + \alpha (T - T_0))$$

$$R_0 = \frac{\Delta V}{I_0} = \frac{120}{1,8} = 66,7 \Omega$$

$$R = \frac{\Delta V}{I} = \frac{120}{1,53} = 78,4 \Omega$$

$$\text{Dara, } \frac{120}{1,53} = \frac{120}{1,8} (1 + \alpha (T - 20))$$

$$T = \frac{\frac{1,8}{1,53} - 1}{0,4 \times 10^{-3}} + 20$$

$$T = 461^\circ\text{C}$$

$$13) \quad R = 5,6 \Omega \quad \Delta V = IR \quad (\Rightarrow I = \frac{\Delta V}{R})$$

$$r = R_{\text{int}} = 0,20 \Omega$$

$$\Delta V = 10 \text{ V} \quad (\Rightarrow I = \frac{10}{5,6} = 1,79 \text{ A})$$

$$\Delta V = E - Ir$$

$$120 = E - 1,79 \times 0,20 \quad (\Rightarrow E = 10,4 \text{ V})$$

$$14) \quad E = 12,6 \text{ V} \quad a) \quad I = \frac{E}{r + R} = \frac{12,6}{0,080 + 5,0} = 2,48 \text{ A}$$

$$r = 0,080 \Omega$$

$$\Delta V = IR = 2,48 \times 5 = 12,4 \text{ V}$$

$$R = 5,0 \Omega$$

$$b) \quad I = 35 \text{ A} \quad I_{\text{extern}} = I_{\text{fiktiv}} \pm 35,0$$

* Dara der Spannung: $\underbrace{I_b r + I_f R = E}_{(1)}$


$$12,6 = (I_f + 35) 0,08 + I_f \times 5 \quad (\Rightarrow 12,6 = 5,08 I_f + 2,8 \quad (\Rightarrow$$

$$\Rightarrow I_f = 1,93 \text{ A}$$

$$\log \Delta V = IR = 1,93 \times 5 = 9,65 \text{ V}$$

(15) $P = 75 \text{ W}$
 $\Delta V = 220 \text{ V}$

$R = 0,80 \Omega$
 $IR = \Delta V$

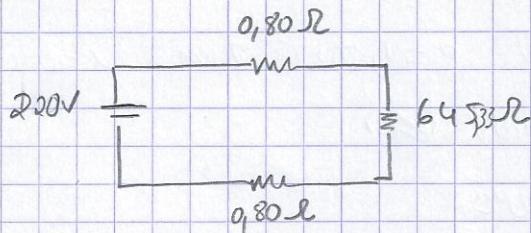

$$P = I \Delta V \Rightarrow P = \frac{(\Delta V)^2}{R} \Leftrightarrow R = \frac{220^2}{75} = 645,33 \Omega$$

Na realidade, $R_{\text{eq}} = 0,80 + 0,80 + 645,33 = 646,43 \Omega$

$$P = \frac{(\Delta V)^2}{R} = \frac{220^2}{646,43} = 74,8 \text{ W}$$

(16) $P_{\text{max}} = 25 \text{ W}$

a) 1º determinar a I_{max}

$$P = I_{\text{max}}^2 \times R$$

$$25 = I^2 \times 100 \Rightarrow I = 0,5 \text{ A}$$

Mas, $R_{\text{eq}} = \frac{100 \times 100}{100+100} = 50 \Omega$ 61, a ✓

$$R_{\text{eq}} = 100 + 50 = 150 \Omega$$


Logo, $\Delta V_{\text{max}} = R_{\text{eq}} I_{\text{max}} = 150 \times 0,5 = 75 \text{ V}$

b) $P_1 = I \Delta V = 0,5 \times 75 = 37,5 \text{ W}$ Potência total

$$P_1 = 25 \text{ W}$$

$$P_2 = P_3 = \frac{37,5 - 25}{2} = 6,25 \text{ W}$$

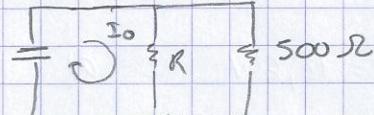17) $\frac{I_0}{I} = 3$
 $R = 500 \Omega // R$




$$\Delta V = I_0 R$$

$$\Delta V = I \left(\frac{R * 500}{R + 500} \right) \quad \left\{ \Leftrightarrow I_0 R = 3 I \left(\frac{500 R}{500 + R} \right) \right.$$

$$\Leftrightarrow 500 + R = 1500 \Rightarrow R = 1000 \Omega$$

(4)

18)

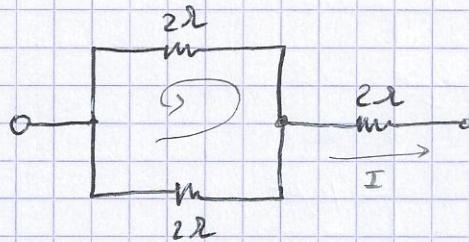

Answers

$$\beta = 32 \text{ W}$$

$$R_{\text{eq}} = \frac{2 \times 2}{2+2} = 1 \text{ ohm} \Rightarrow R = 1 + 2 = 3 \text{ ohms}$$

de cada R:

$$\beta = I^2 R \Leftrightarrow 32 = I^2 \times 2 \Leftrightarrow I = 4 \text{ A}$$


loop me combinap:

$$\beta = I^2 R_{\text{eq}} \Leftrightarrow \beta = 4^2 \times 3 = 48 \text{ W}$$

$$19) R = 1 \text{ M}\Omega = 1 \times 10^6 \text{ ohms}$$

$$C = 5 \mu\text{F} = 5 \times 10^{-6} \text{ F}$$

$$E = 30 \text{ V}$$

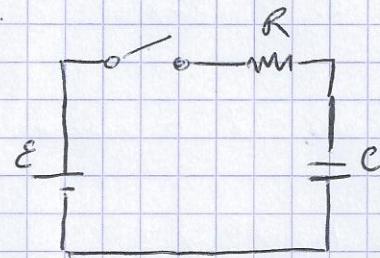

20)


$$a) \tau = RC = 1 \times 10^6 \times 5 \times 10^{-6} = 5 \text{ s}$$

$$b) Q = CE = 5 \times 10^{-6} \times 30 = 150 \times 10^{-6} \text{ C}$$

$$c) t=0 \rightarrow I(t) = I_0 e^{-t/\tau}$$

$$I_0 = \frac{E}{R} = \frac{30}{1 \times 10^6} = 30 \times 10^{-6} \text{ A}$$
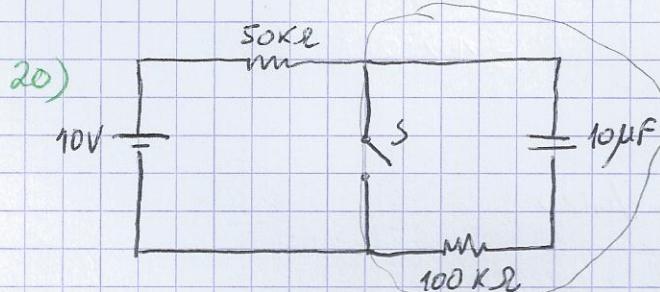
$$I(10) = +30 \times 10^{-6} e^{-10} = +4,1 \times 10^{-6} \text{ A}$$



$$a) \tau = RC$$

$$\text{Antes: } R_{\text{eq}} = 100 + 50 = 150 \text{ k}\Omega$$

$$\tau = 150 \times 10^3 \times 10 \times 10^{-6} = 1,5 \text{ s}$$

$$\text{depois: } R = 100 \text{ k}\Omega \quad \tau = 100 \times 10^3 \times 10 \times 10^{-6} = 1,0 \text{ s}$$


$$b) I = I_{\text{balance}} + I_{RC} \quad (\Rightarrow)$$

$$I_0 = \frac{E}{R} = \frac{10}{100 \times 10^3} = 1 \times 10^{-4} \text{ A}$$

$$I = 2 \times 10^{-4} + 1 \times 10^{-4} e^{-t/1}$$

(comprimento!)
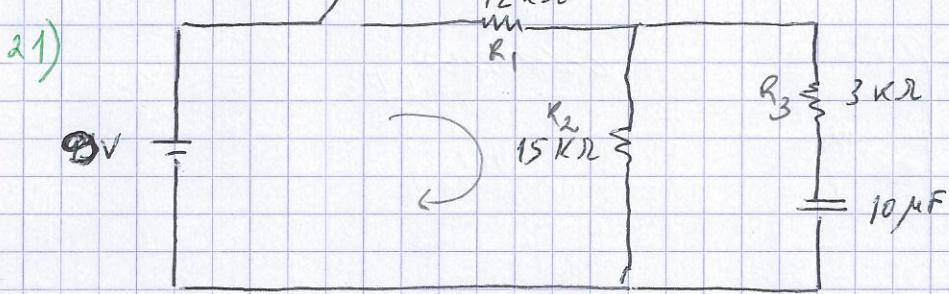
$$I_{\text{balance}} = \frac{10}{50 \times 10^3} = 2 \times 10^{-4} \text{ A} \quad e \quad R_C = 100$$



a) No há corrente no circuito AC após estabilização

$$\text{Logo, } I_3 = 0 \text{ A}$$

$$\text{Logo, } R_{\text{eq}} = R_1 + R_2 = 12 + 15 = 27 \text{ kΩ} \quad , \text{A inversão é a de metade em } R_1 \text{ e } R_2$$

$$\text{Logo, } I = \frac{E}{R_{\text{eq}}} = \frac{9}{27 \times 10^3} = \frac{1}{3} \times 10^{-3} \text{ A} \quad (\frac{1}{3} \text{ mA})$$

b) O potencial em C é o mesmo que em R₂, não há corrente em R₃

$$\text{Logo, } Q = C \Delta V = 10 \times 10^{-6} \times I R_2 = 10 \times 10^{-6} \times \frac{1}{3} \times 10^{-3} \times 15 \times 10^3$$

$$\Rightarrow Q = 5 \times 10^{-5} \text{ C}$$

$$\text{c) } I = I_0 e^{-t/RC} \quad \cancel{\text{X}}$$

$$I = (R_2 + R_3) C = 0,180 \rightarrow$$

$$I_0 = \frac{IR_2}{R_2 + R_3} = \frac{\frac{1}{3} \times 10^{-3} \times 15 \times 10^3}{18 \times 10^3} = 2,78 \times 10^{-4} \text{ A}$$

$$\text{Logo, } I(t) = 2,78 \times 10^{-4} \times e^{-t/0,180} \quad (\text{A})$$

$$d) \Delta V_f = \frac{1}{5} \Delta V \Rightarrow Q_f = C \times \frac{1}{5} \Delta V = 1 \times 10^{-5} \text{ C}$$

$$Q_f(t) = Q_i e^{-t/0,180}$$

$$1 \times 10^{-5} = 5 \times 10^{-5} e^{-t/0,180}$$

$$\frac{1}{5} = e^{-t/0,180}$$

$$-\frac{t}{0,180} = \ln\left(\frac{1}{5}\right) \Rightarrow t = 0,290 \text{ s}$$

(5)

22) $E_2 = 3$

$E_{\max} = 2 \times 10^8 \text{ V/m}$

$C = 0,25 \mu\text{F}$

$\Delta V_{\max} = 4000 \text{ V}$

$A = ?$

$C = \epsilon_0 \times \epsilon_r \times \frac{A}{d}$


$\Delta V = Ed$

$4000 = 2 \times 10^8 \times d \Rightarrow d = 2 \times 10^{-5} \text{ m}$

\log

$0,25 \times 10^{-6} = 8,85 \times 10^{-12} \times 3 \times \frac{A}{2 \times 10^{-5}}$

$\Rightarrow A = 0,188 \text{ m}^2$

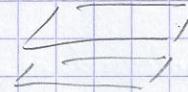

23) d { placa
 A

S { condensador
 A

Dois condensadores em série

$a + d + b = S$

$$C = \frac{\epsilon_0 \times C_b}{C_a + C_b} = \frac{\epsilon_0 \frac{A}{a} \times \epsilon_0 \frac{A}{b}}{\epsilon_0 \frac{A}{a} + \epsilon_0 \frac{A}{b}} = \frac{\epsilon_0^2 A^2 \times \frac{1}{ab}}{\epsilon_0 A \left(\frac{1}{a} + \frac{1}{b} \right)} = \\ = \epsilon_0 A \times \frac{\frac{1}{ab}}{\frac{b+a}{ab}} = \frac{\epsilon_0 A}{a+b} = \epsilon_0 \frac{A}{S-d}$$

24) q_0

$C_i = \epsilon_0 \times \frac{A}{d}$

$C_f = \epsilon \epsilon_0 \times \frac{A}{d}$

$+q$

$Q = C \Delta V \Rightarrow \Delta V = \frac{Q}{C}$

$\frac{q_0}{\epsilon_0 \frac{A}{d}} = \frac{q + q_0}{\epsilon_2 \epsilon_0 \times \frac{A}{d}} \Rightarrow \epsilon_2 = \frac{q + q_0}{q_0} \Leftrightarrow$

$\Rightarrow \epsilon_2 = 1 + \frac{q}{q_0}$

25) $C = 3 \text{ pF}$

$Q = C \times \Delta V = 2,4 \times 10^{-9}$

$\Delta V = 800 \text{ V}$


$Q_i = 6 \times 10^{-12} \times 200 = 1,2 \times 10^{-9}$

$C_i = 6 \text{ pF}$

$\frac{\Delta V}{\Delta V_i} = 4$

$\frac{Q}{Q_1} = 2$

$\Delta V_f = 200 \text{ V}$

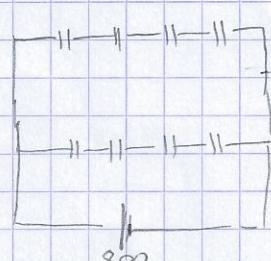


$C_f = \left(\frac{1}{6} \times 4 \right)^{-1} = 1,5 + = 3 \text{ } \checkmark$

$C_g = \left(\frac{1}{6} \times 4 \right)^{-1} = 1,5$

$Q = 1,5 \times 800 + 1,5 \times 800 = 2,4 \times 10^{-9} \text{ C} \checkmark$

26) $\# \text{ undeselected} = 10$

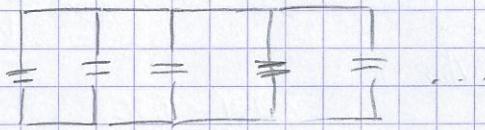

$$C = 500 \mu F$$

$$\Delta V = 800 V$$

$$C_{eq} = 10 \times 500 \times 10^{-6} = 5 \times 10^{-3} F$$

$$\Delta Q = C \Delta V = 5 \times 10^{-3} \times 800 = 4 C \text{ total} \Rightarrow Q_i = 0,4 C$$

$$\text{Series: } C_{eq} = \left(\frac{10}{500 \times 10^{-6}} \right)^{-1} = 5 \times 10^{-3} F \quad \text{parecada}$$

$$\text{loop } \Delta V = \frac{Q}{C} = \frac{0,4}{5 \times 10^{-3}} = 8 \times 10^3 V \quad \checkmark$$